
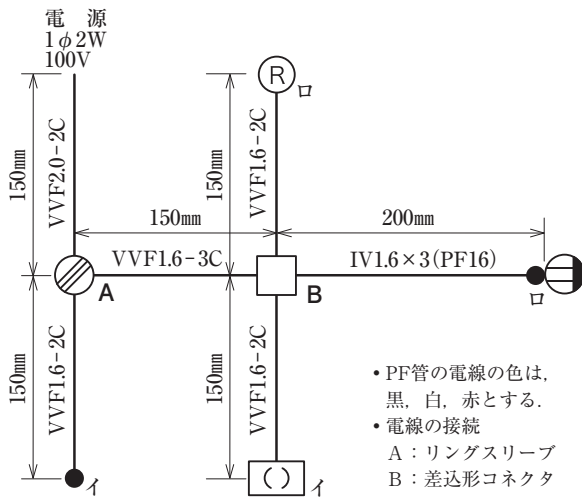


第2編③_例題7_p109

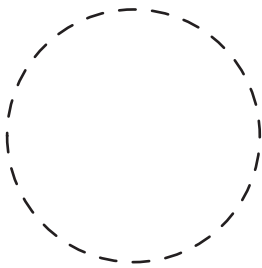


電 源
1φ2W
100V
黒 | | 白

(R) □



A

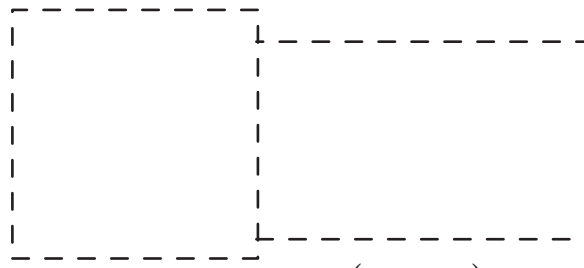

B

(PF16)

